
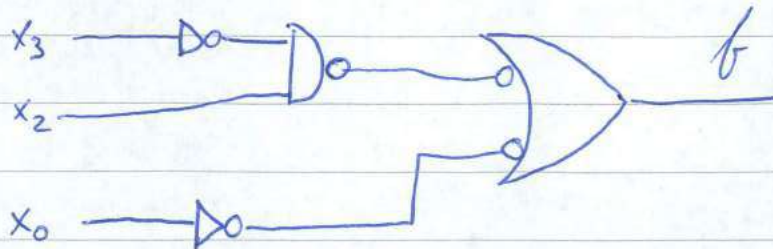


A.1

$$f(x_3, x_2, x_1, x_0) = \sum(0, 2, 4, 5, 6, 7) + d(8, 10, 12, 14).$$


	$x_1 x_0$			
	00	01	11	10
$x_3 x_2$	00	1		1
	01	1	1	1
	11	-		-
	10	-		-
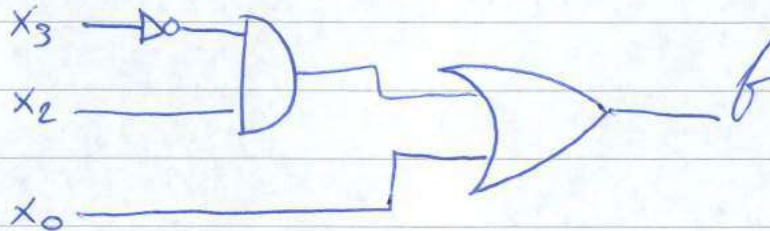
$$f(x_3, x_2, x_1, x_0) = \overline{x_0} + \overline{x_3} \cdot x_2$$



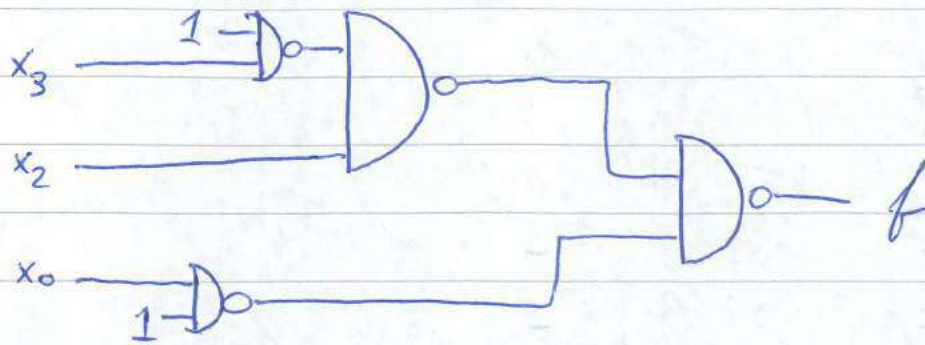
$$x \text{ --- } \neg \text{ --- } Y \rightsquigarrow x \text{ --- } \neg \text{ --- } Y \quad (\text{or } x \text{ --- } \neg \text{ --- } Y)$$





A.2

State diagram:

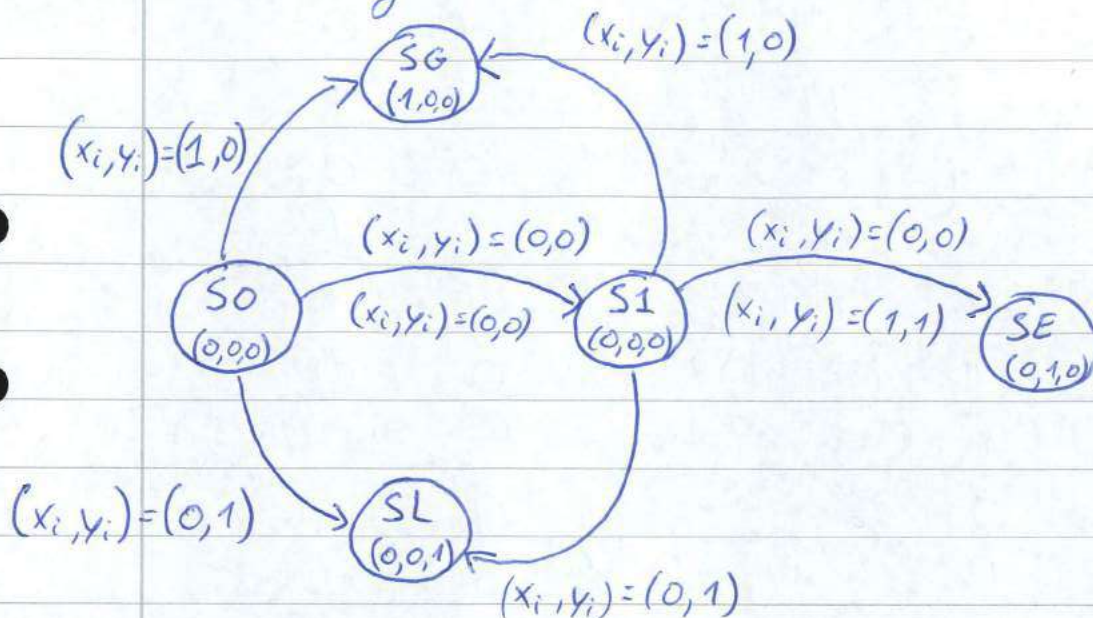


State coding (and output):

State	q_2	q_1	q_0	z_2	z_1	z_0
S0	0	0	0	0	0	0
S1	0	0	1	0	0	0
SG	1	1	0	1	0	0
SE	1	0	0	0	1	0
SL	1	0	1	0	0	1

State transitions:

q_2	q_1	q_0	x_i	y_i	q_2^+	q_1^+	q_0^+
0	0	0	0	0	0	0	1
0	0	0	0	1	1	0	1
0	0	0	1	0	1	1	0
0	0	0	1	1	0	0	1
0	0	1	0	0	1	0	0
0	0	1	0	1	1	0	1
0	0	1	1	0	1	1	0
0	0	1	1	1	1	0	0
-	-	-	-	-	-	-	-
1	0	0	-	-	1	0	0
1	0	1	-	-	1	0	1
1	1	0	-	-	1	1	0
-	-	-	-	-	-	-	-

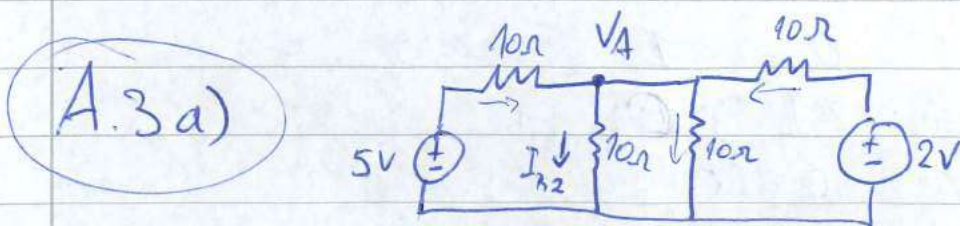Implemented as a Moore machine with 3 D Flip-Flops.




We can use the method of potentials (Kirchhoff's current law)

$$\frac{5-V_A}{R_1} - \frac{V_A}{R_2} - \frac{V_A}{R_3} + \frac{2-V_A}{R_4} = 0 \quad (\Rightarrow) \quad \frac{1}{10}(7 - 4V_A) = 0 \quad (\Rightarrow) \quad V_A = \frac{7}{4} \text{ V}$$

$$I_{R_2} = \frac{V_A}{R_2} = \frac{7}{40} \text{ A}$$

A.3.b)

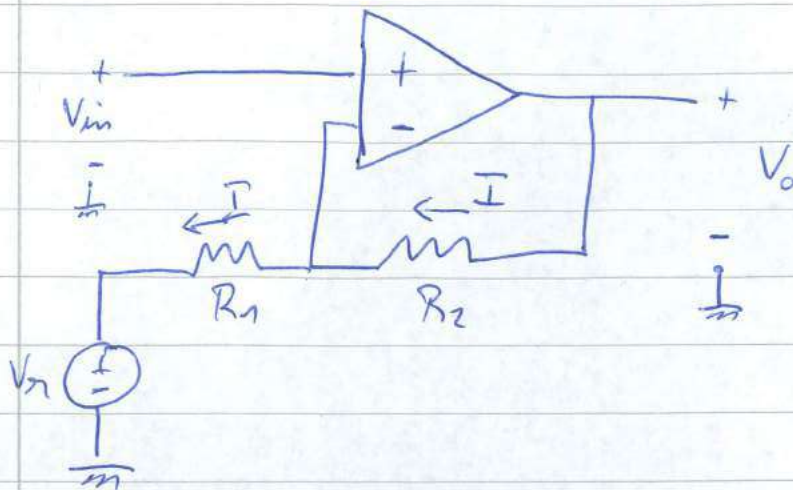

$$V_o = V_{in} + R_2 I$$

$$I = \frac{V_{in} - V_o}{R_1}$$


\Rightarrow

$$V_o = V_{in} + \frac{R_2}{R_1} (V_{in} - V_o)$$

$$\therefore V_o = \left(1 + \frac{R_2}{R_1}\right) V_{in} - \frac{R_2}{R_1} V_o$$

$$= 3V_{in} - 4$$


A.4

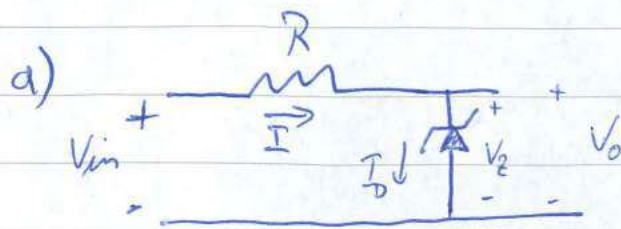

$$I_D = I = \frac{V_{in} - V_Z}{R} = \frac{9 - 5}{R}$$


$$I_D < 20 \text{ mA} (=) \quad \frac{4}{R} < 20 \times 10^{-3} (=)$$
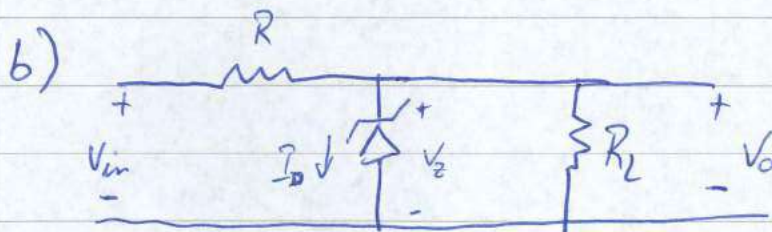
$$R > \frac{4}{20} \times 10^3 = 200 \Omega$$



$$V_o = V_Z = \begin{cases} 5V, & \text{if } I_D > 0 \quad (\text{Reverse conduction}) \\ \frac{R_L}{R+R_L} V_{in}, & \text{if } I_D = 0 \quad (\text{No conduction}) \end{cases}$$

$\therefore I_D > 0$

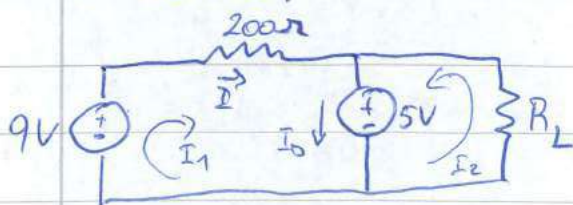

$$\begin{cases} 9 - 200I_1 - 5 = 0 \\ -R_L I_2 - 5 = 0 \\ I_D = I_1 + I_2 \end{cases} \quad (=) \quad \begin{cases} I_1 = \frac{4}{200} = 20 \text{ mA} \\ I_2 = -\frac{5}{R_L} \\ I_D = 0.02 - \frac{5}{R_L} \end{cases}$$

$$I_D > 0 \quad (=) \quad 0.02 > \frac{5}{R_L} \quad (=) \quad R_L > \frac{5}{0.02} = 250 \Omega$$


A.5

$$V_{in}(t) = 3 \sin \left(20 \times 10^3 \pi t - \frac{\pi}{2} \right) = \\ = \text{Im}(V_{in}) = \text{Im} \left(3 e^{-j\frac{\pi}{2}} e^{j2 \times 10^4 \pi t} \right)$$

$$V_{in} = 3 e^{-j\frac{\pi}{2}}$$

$$\omega = 2 \times 10^4 \pi \text{ rad/s}$$

(the phasor of the complex voltage)

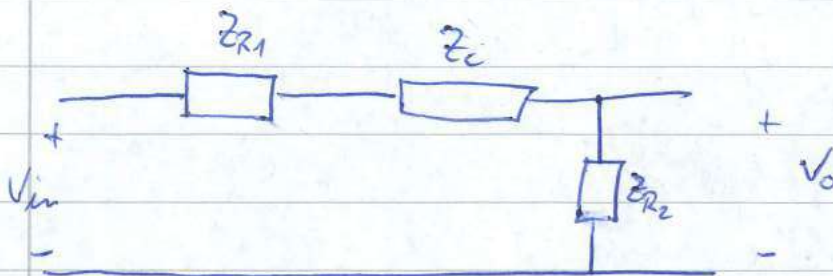

$$Z_{R1} = R_1, \quad Z_{R2} = R_2, \quad Z_C = \frac{1}{j\omega C}$$

$$V_o = \frac{Z_{R2}}{Z_{R1} + Z_{R2} + Z_C} V_{in} = \frac{R_2}{R_1 + R_2 + \frac{1}{j\omega C}} V_{in} =$$

$$= \frac{j\omega R_2 C}{1 + j\omega(R_1 + R_2)C} V_{in}$$

$$\begin{aligned} R_1 &= R_2 = 500 \, \Omega \\ C &= 0.1 \, \mu\text{F} = 10^{-7} \, \text{F} \\ \omega &= 2 \times 10^4 \pi \text{ rad/s} \end{aligned}$$

$$V_o = \frac{j 2\pi \times 10^4 \times 500 \times 10^{-7}}{1 + j 2\pi \times 10^4 \times 10^{-7} \times 10^{-7}} V_{in} = \frac{j\pi}{1 + j2\pi} \times V_{in}$$

$$\frac{j\pi}{1 + j2\pi} = \left| \frac{j\pi}{1 + j2\pi} \right| e^{j \arg\left(\frac{j\pi}{1 + j2\pi}\right)}$$

$$\left| \frac{j\pi}{1+j2\pi} \right| = \frac{\pi}{\sqrt{1+4\pi^2}}$$

$$\arg\left(\frac{j\pi}{1+j2\pi}\right) = \frac{\pi}{2} - \arctan(2\pi)$$

$$\therefore V_0 = \frac{j\pi}{1+j2\pi} \times V_{in} = \frac{\pi}{\sqrt{1+4\pi^2}} e^{j\left(\frac{\pi}{2} - \arctan(2\pi)\right)} \times 3 e^{-j\pi/2}$$

$$V_0 = \frac{3\pi}{\sqrt{1+4\pi^2}} e^{-j\arctan(2\pi)}$$

$$V_0(t) = \text{Im}\left(V_0 e^{j2 \times 10^4 \pi t}\right) =$$

$$= \frac{3\pi}{\sqrt{1+4\pi^2}} \sin\left(2 \times 10^4 \pi t - \arctan(2\pi)\right)$$