



UPPSALA
UNIVERSITET



2974058

Försättsblad tentamen / Examination cover

Teknisk- naturvetenskapliga fakulteten /
Faculty of Science and Technology

Kursnamn / Course name

Digitalteknik och elektronik

Kurskod / Course code

1 T E 7 1 7

Provkod / Test code

1 0 0 0

Tentamensdatum / Examination date

Y/Y/Y/Y M/M D/D
2 0 1 9 - 1 0 - 3 1

Anonymkod / Anonymous code

B O - 0 0 6 1 - N X X

2974058



Utskriven 2019-11-22 kl. 14:20:44

Exam: 1TE717 Digital Technologies and Electronics

Date: October 31, 2019

Name / Code:

BO-0061-NXX

Part A.

	A1	A2	A3	A4	A5	Total		
MAX Pts	4	5	9	6	6	30		
Score	3.5	4.5	9	5.5	6	28.5		

Total A: 28.5

Part B.

	B1	B2	B3		Total		
MAX Pts	8	6	6		20		
Score	8	5	—		13		
Bonus Pts							

Total B: 13

Exam Grade:

5

DTE-1TE717, 2019-10-31

A.1

$$f(x_3, x_2, x_1, x_0) = \sum(0, 2, 4, 8, 10) + d(1, 6, 13, 14)$$

x_3	x_2	x_1	x_0	$f(\vec{x})$
0	0	0	0	1
0	0	0	1	X
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	X
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	X
1	1	1	0	X
1	1	1	1	0

Karnaugh:


$x_3 \backslash x_2$	00	01	11	10
00	1	X	0	1
01	1	0	0	X
11	0	X	0	X
10	1	0	0	1

$$f(\vec{x}) = \overline{x}_2 \cdot \overline{x}_0 + \overline{x}_3 \cdot \overline{x}_1 \cdot \overline{x}_0 \quad \left(\text{Minimal Sum of Products} \right)$$

$$\left(\overline{x}_2 + (\overline{x}_3 \cdot \overline{x}_1) \right) \cdot \overline{x}_0 = \left(\overline{x}_2 \cdot (\overline{x}_3 \cdot \overline{x}_1) \right) \cdot \overline{x}_0$$

De Morgan: $\overline{A+B} = \overline{A} \cdot \overline{B}$
 $A = x_2, B = (\overline{x}_3 \cdot \overline{x}_1)$

$$= \overline{\left(x_2 \cdot (\overline{x}_3 \cdot \overline{x}_1) \cdot \overline{x}_0 \right)} = \overline{\overline{x}_0 \cdot \left(x_2 \cdot (\overline{x}_3 \cdot \overline{x}_1) \right)}$$

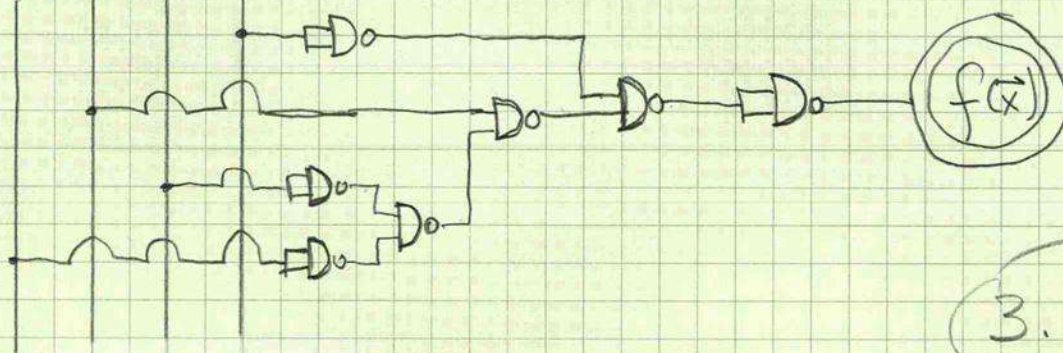 $x_3 \quad x_2 \quad x_1 \quad x_0$ 


3.5

A.2

1. A state diagram:

2&3. State coding and truth table:

	q_5	q_4	q_3	q_2	q_1	x	q_5^+	q_4^+	q_3^+	q_2^+	q_1^+	y
S_0	0	0	0	0	0	0	0	0	0	0	1	0
	0	0	0	0	0	1	0	0	0	0	0	0
S_1	0	0	0	0	1	0	0	0	0	0	1	0
	0	0	0	0	1	1	0	0	0	1	0	0
S_2	0	0	0	1	0	0	0	0	1	0	0	0
	0	0	0	1	0	1	0	0	0	0	0	0
S_3	0	0	1	0	0	0	0	0	0	0	1	0
	0	0	1	0	0	1	0	1	0	0	0	0
S_4	0	1	0	0	0	0	1	0	0	0	0	0
	0	1	0	0	0	1	0	0	0	0	0	0
S_5	1	0	0	0	0	0	0	0	0	0	1	1
	1	0	0	0	0	1	0	0	0	0	0	1

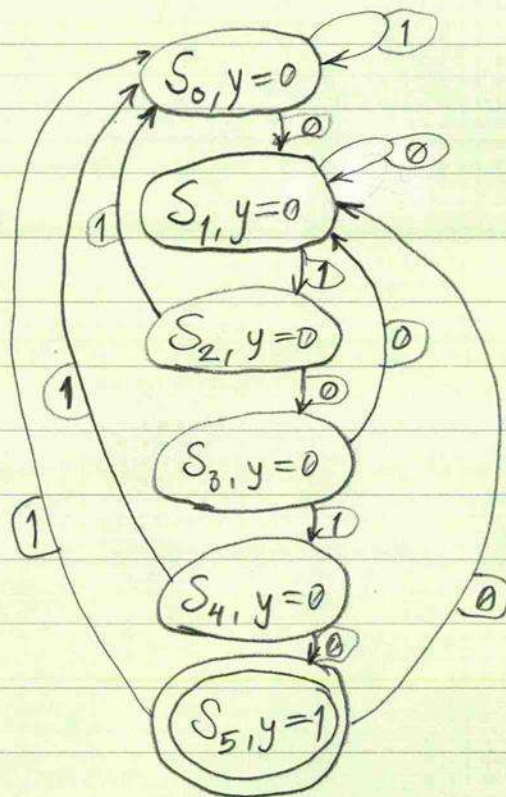


This is a Moore machine. ✓
It needs 5 flip-flops,
one for each state variable. ✓

All other lines in the truth table
will have don't care for q_i^+ , $i=1, \dots, 5$

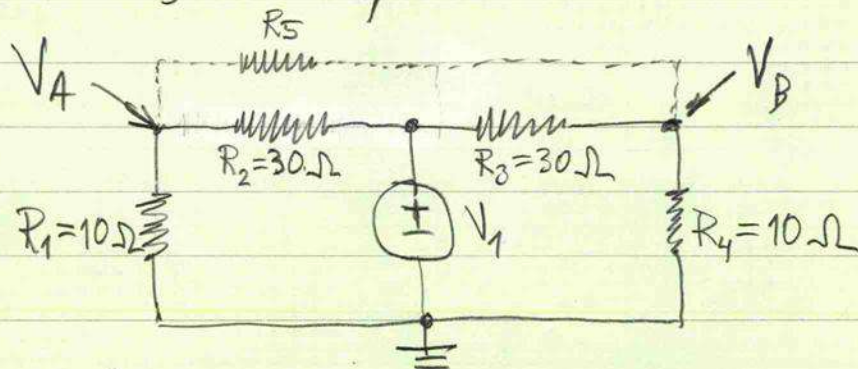4.5


1TE717, 2019-10-31

A.3 a) Since there is only one voltage source, and since $R_2 = R_3$ and $R_1 = R_4$, the circuit is completely symmetric. Because of this, the potential between R_1 and R_2 will be the same as the potential between R_3 and R_4 :




Because of symmetry, V_A will equal V_B .
As a result, no current will flow through R_5 .

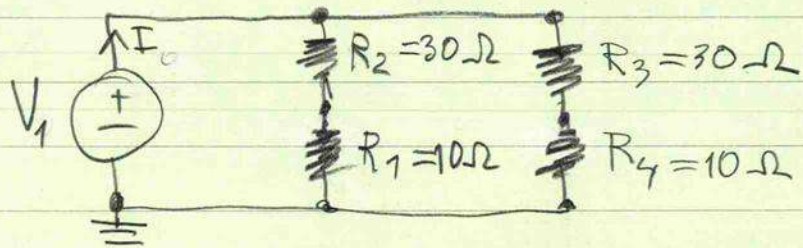
The whole circuit may now be replaced by one looking as:



or

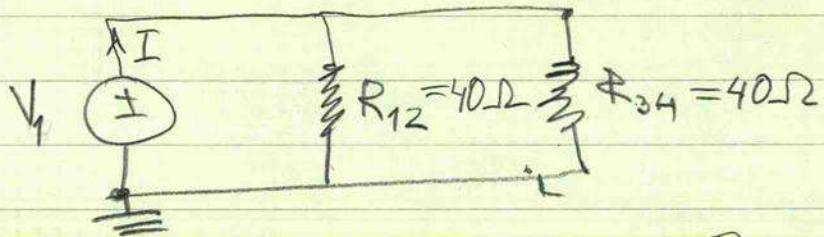

or

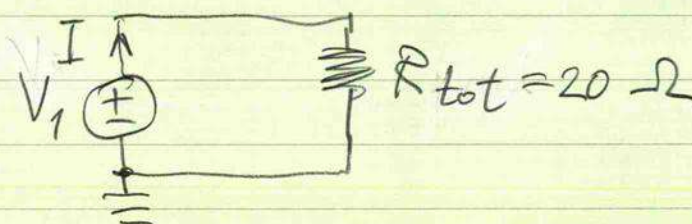


} This answers
P.1a)
as well.

Answer: the current passing through the voltage source goes upwards and is $5V/20\Omega = 0.25A$.

1.TE 717, 2019-10-31

A.3b)

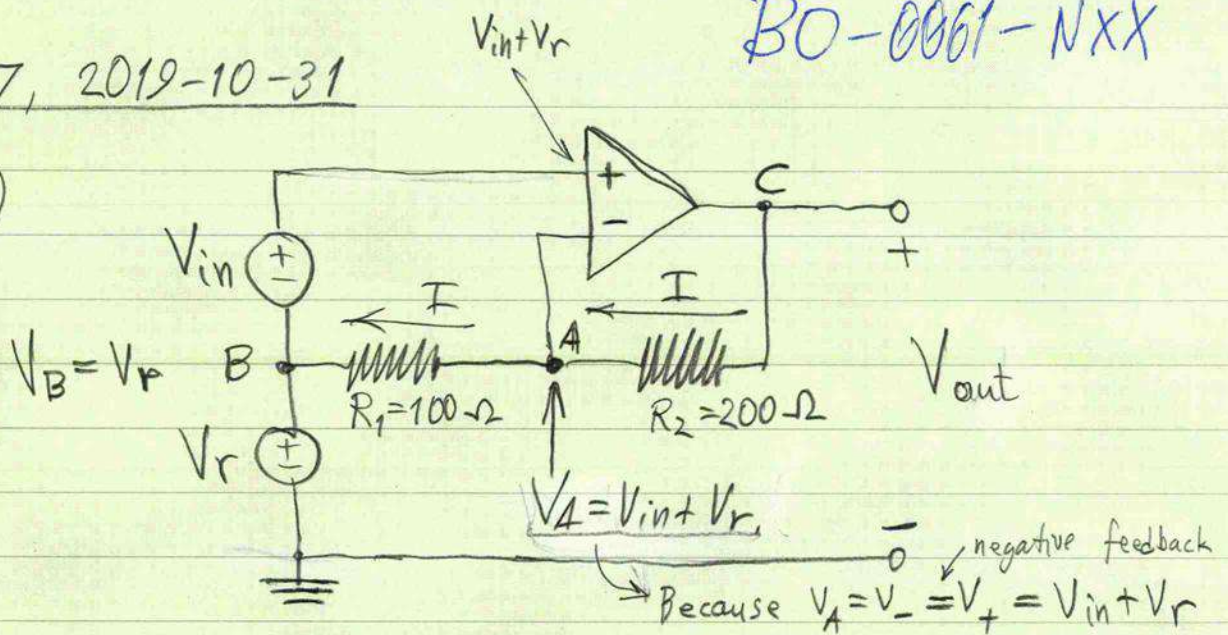

Since the OpAmp is ideal, and since it gets negative feedback (through R_2), the voltage drop from C to A is $\frac{R_2}{R_1}$ times the voltage drop from A to B:

Also $I_+ = I_- = 0$ (because the OpAmp is ideal and has negative feedback)

Hence the current flowing (leftwards) through R_1 is the same as the current flowing (also leftwards) through R_2 :

$$\frac{V_{in}}{R_1} = \frac{V_{out} - V_{in} - V_r}{R_2} \Rightarrow \frac{V_{out}}{R_2} = \frac{V_{in}}{R_1} + \frac{V_{in}}{R_2} + \frac{V_r}{R_2}$$

$$\text{Or, } V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in} + V_r = (1+2) \cdot 3V + 2V = \underline{\underline{11V.}}$$

$$\text{The current is } \frac{3V}{100\Omega} = 30 \text{ mA}$$

$$\frac{R_2}{R_1} = 2, V_{in} = 3V, V_r = 2V$$

Answer: The expression for the output voltage V_o is

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_{in} + V_r \quad \text{The current passing through } R_2 \text{ is } (11-3)V/200\Omega = 30 \text{ mA} \quad \underline{\text{leftwards}} \quad \checkmark$$

1TE717, 2019-10-31

A.4 a) $R_E = 50 \Omega \Rightarrow \underline{I_E} = (V_{in} - V_{BE}) / R_E = (5.6 - 0.6) V / 50 \Omega$
 $= 5 V / 50 \Omega = 0.1 A = \underline{100 mA} \checkmark$

Since (by definition of β) $I_C = \beta I_B$, and since $I_E = I_B + I_C$ it follows that $I_E = I_B + \beta I_B = (1 + \beta) I_B$ and hence that

$\underline{I_B} = (\beta + 1)^{-1} I_E = 301^{-1} \cdot 100 mA = \underline{332 \mu A} \checkmark$

And since $\underline{I_C} = I_E - I_B = 100 mA - 0.33 mA = \underline{99.67 mA} \checkmark$

The voltage drop over the resistor R is $R I_C = 0.1 k\Omega \cdot 99.7 mA$
 $= \underline{9.97 V}$

The V_{CE} becomes the residual voltage

drop over the transistor: $V_{CE} = V_s - V_D - R I_C - R_E I_E \checkmark$
 $= (24 - 2 - 9.97 - 5.0) V = \underline{7.03 V}$

Answer: $V_{CE} = 7.03 V$; $I_E = 100 mA$; $I_C = 99.7 mA$; $I_B = 332 \mu A \checkmark$

{ and the BJT is in its cut-off region, meaning the transistor
 is (partly) off. \times 2.5

A.4 b) Saturation mode $\Rightarrow V_{CE} = 0.2 V$ so the voltage drop over R must be $(24 - 5 - 2 - 0.2) V = 16.8 V$ which means the current flowing through R must be big enough, $I_C = (16.8 V) / 0.1 k\Omega = \underline{168 mA}$
 $\Rightarrow I_{B, \min} = 168 mA / 300 = 560 \mu A$. Since $I_E = (\beta + 1) I_B$ it follows that $I_{E, \min} = 301 \cdot 560 \mu A = 168.56 mA$

Finally, for I_E not to be too small, R_E must not be too large, $R_{E, \max} = 5 V / 168.56 mA = \underline{29.66 \Omega} \checkmark$

Answer: for the transistor to be in saturation mode, the resistor R_E must be no larger than $\underline{29 \Omega}$.

32

1TE717, 2019-10-31

BO-0061-NXX

A.5 $V_{in}(t) = 3 \sin(10000\pi t + \frac{\pi}{2}) = \text{Im}(\Phi_{in} e^{j\omega t})$
 where $\Phi_{in} = A_{in} e^{j\psi}$, $A_{in} = 3V$, $\psi = \arg(\Phi_{in}) = \frac{\pi}{2}$, $\omega = 10\pi \text{ krad/sec}$

$\Phi_{out} = H(j\omega) \Phi_{in}(j\omega)$, where Φ_{in} is as above and

$H(j\omega) = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} \cdot \frac{j\omega C}{j\omega C} = \frac{j\omega RC}{1 - \omega^2 LC + j\omega RC} \cdot \frac{1 - \omega^2 LC - j\omega RC}{1 - \omega^2 LC - j\omega RC}$

$H(j\omega) = \frac{(\omega RC)^2 + j\omega RC(1 - \omega^2 LC)}{(1 - \omega^2 LC)^2 + (\omega RC)^2} = a + j b$

where
 $a = \frac{(\omega RC)^2}{(1 - \omega^2 LC)^2 + (\omega RC)^2}$ $C = 1 \mu F$
 $L = 1 \text{ mH}$
 $R = 0.05 \text{ k}\Omega$
 $b = \frac{\omega RC(1 - \omega^2 LC)}{(1 - \omega^2 LC)^2 + (\omega RC)^2}$ $\omega = 10\pi \text{ krad/sec}$
 $\arg(H(j\omega)) = \arctan \frac{b}{a}$ (*)

With numbers inserted into (*):

$a \approx 0.999931$ $b \approx 0.008301$

$|H(j\omega)| = \sqrt{a^2 + b^2} \approx 0.999966$

$\arctan \frac{b}{a} \approx 0.008301$

$\arg(\Phi_{out}(j\omega)) = \arg(H(j\omega)) + \arg(\Phi_{in}) = 0.008301 + \frac{\pi}{2} \approx 1.5791$ ✓

$|\Phi_{out}(j\omega)| = |H(j\omega)| \cdot A_{in} \approx 2.999897 V$ ✓

Recall that $V_{out}(t) = \text{Im}(\Phi_{out} e^{j\omega t})$

Answer: $V_{out}(t) = 2.9999 \sin(10000\pi t + 1.5791)$ ✓

Low-pass? High-pass? Band-pass? Band-stop?

$H(s) = H(j\omega) = \frac{(j\omega)RC}{1 + (j\omega)^2 LC + (j\omega)RC} \xrightarrow{s=j\omega} \frac{sRC}{1 + sRC + s^2 LC} \Rightarrow H(0) = \frac{0 \cdot RC}{1 + 0 + 0} = 0$

For $s \rightarrow \infty$, rewrite $H(s)$ as $H(s) = \frac{\frac{1}{s^2} RC}{\frac{1}{s^2} + \frac{1}{s} RC + LC}$

from which it is clear that $H(s) \rightarrow 0$ as $s \rightarrow \infty$


00 This is a BAND-PASS (6p)

BO-0061-NXX

B.1 a) See A.3 a) ! ✓


(3r)

b)

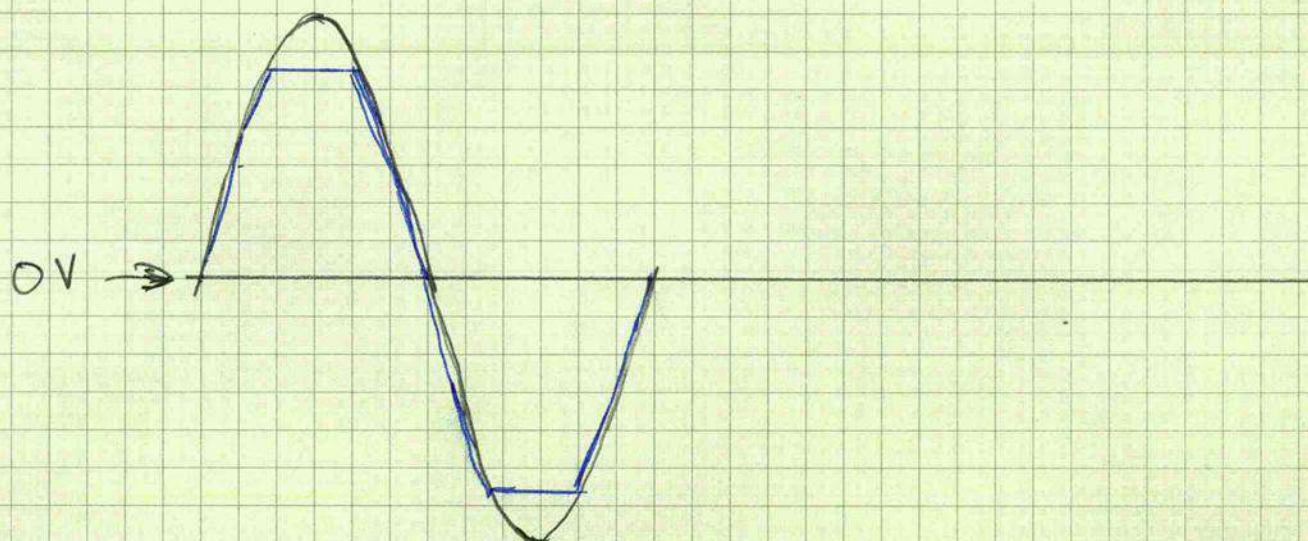

✓ - black: input signal
- blue: output signal

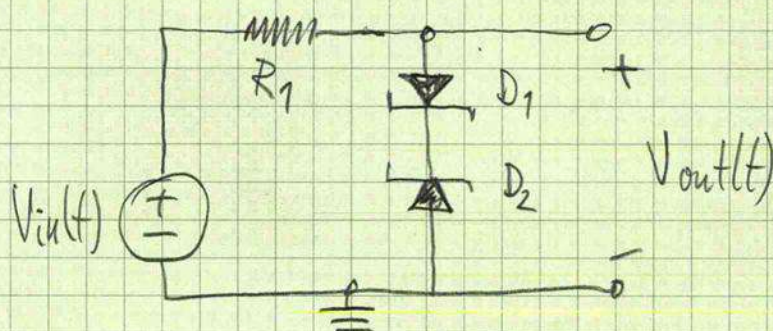
} The diodes will cut the input signal at $\pm 5.5 \text{ V}$ ✓



The reason is that the diodes will start conducting when... ✓

TIME IS OUT!

(5p)

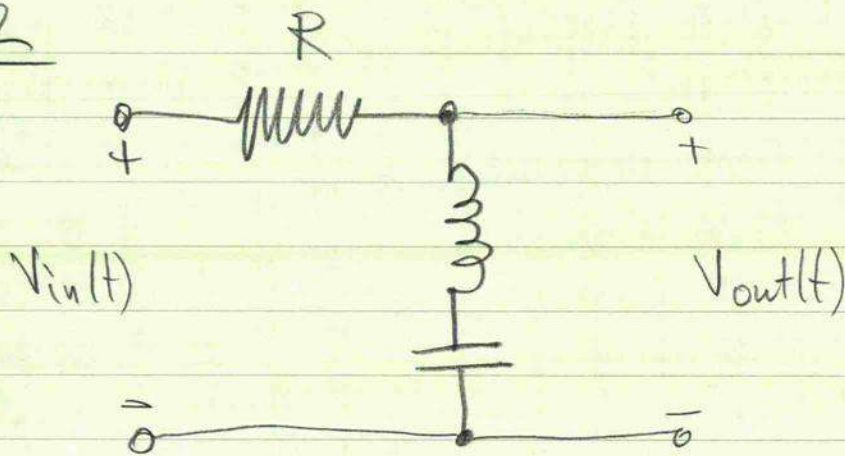B.2

↑ This is a passive band-stop. I don't have time to explain why, but it is the inverse of the output signal in Figure 4. ✓
 By doing similar calculations as in A.5 I could show that: for the transactional function $H(j\omega)$:

$$\left. \begin{array}{l} \checkmark |H(0)| = 1 \\ \checkmark \text{ and } |H(\infty)| = 1 \end{array} \right\} \text{ AND for some frequency } \omega^* \text{ in between, } |H(j\omega^*)| = 0$$

(5p)